Quiz 6

 $V_g = 40 \text{m V}$ Find $V_o(t)$ $R_a = 400 \text{k}$ $R_1 = 500 \text{k}$ $R_b = 400 \text{k}$ $R_2 = 2.5 \times 106$ $C_1 = 250 \times 10^9$ $C_2 = 100 \times 10^9$

particular solution: $V_{01}(\infty) = V_{01}(\frac{-Ra}{R_{1}}) = \frac{40}{1000}(\frac{-4\times10^{5}}{5\times10^{5}}) = 0.04\times(-0.8) = -0.032$

=> Voi(t) = -0.032+Be-at

 $T_1 = 5 \times 10^5 \times 250 \times 10^{-9} = 0.125$ $T_2 = 2.5 \times 10^6 \times 100 \times 10^{-9} = 0.25$

 $\frac{d^{2}V_{o}}{dt^{2}} + (8+4)\frac{dV_{o}}{dt} + (32)V_{o} = \frac{0.04}{4\times10^{5}\times250\times10^{-9}\times400\times10^{3}\times100\times10^{-9}}$

 $=\frac{d^2V_0}{dt^2+12}\frac{dV_0}{dt}+32V_0=10$

 $X = (R_1 + R_2)^2 C_2^2 - 4R_1 C_1 R_2 C_2$ $= (3M)^2 (10^{-14}) - 125 \times 10^{10} \times 25000 \times 10^{-18}$ $= 9 \times 10^{-12} - 0.03125$

[underdamped]