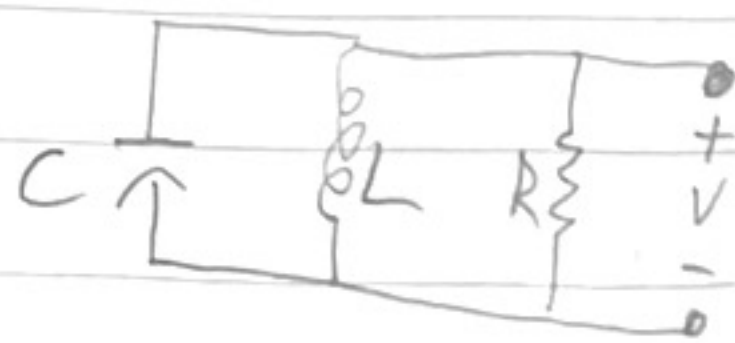


natural response: no voltage source

Natural response & Step response of Parallel RLC circuit

① voltage is preferred because it's continuous all the time  
voltage is same for all three components, and makes  
us easier to calculate branch current



$$I_C + I_L + I_R = 0$$

$$\Rightarrow C \frac{dV(t)}{dt} + \frac{1}{L} \int_0^t V(x) dx + I_0 + \frac{V(t)}{R} = 0$$

$$\Rightarrow \frac{d^2 V(t)}{dt^2} + \frac{1}{LC} V(t) + \frac{1}{RC} \frac{dV(t)}{dt} = 0 \text{ (standard form)}$$

Some qualities of this standard form: ① second order ② Homogeneous

③ Ordinary diff equation ④ has constant coefficients

Which can also be  $V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$  or  $s^2 + (1/RC)s + (1/LC) = 0$

Where  $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$  &  $\alpha = \frac{1}{2RC}$  &  $\omega_0 = \sqrt{\frac{1}{LC}}$

So the form of  $s_1$  &  $s_2$  depends on  $\sqrt{\alpha^2 - \omega_0^2}$ :

$\alpha^2 > \omega_0^2$ : overdamped,  $V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

$\alpha^2 < \omega_0^2$ : underdamped,  $V(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$   
And  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$

$\alpha^2 = \omega_0^2$ : Critical damped:  $s_1, s_2 = -\alpha$ ,  $V(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$

For step response:  $\frac{d^2 I_L}{dt^2} + \frac{1}{RC} \frac{dI_L}{dt} + \frac{I_L}{LC} = \frac{I}{LC}$  Char equation:  $s^2 + (1/RC)s + (1/LC) = 0$

$I_L(t) = I_F + I_N$  where  $I_F$  is particular solution &  $I_N$  is homogeneous

Inductor current is preferred because it's only component, final value isn't zero.

$\alpha = \frac{1}{2RC}$ ,  $\omega_0 = \sqrt{\frac{1}{LC}}$   $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$


$\alpha^2 > \omega_0^2$   $I_L(t) = I_F + A'_1 e^{s_1 t} + A'_2 e^{s_2 t}, t \geq 0$

$\alpha^2 < \omega_0^2$   $I_L(t) = I_F + B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t, t \geq 0$

$\alpha^2 = \omega_0^2$   $I_L(t) = I_F + D'_1 t e^{-\alpha t} + D'_2 e^{-\alpha t}, t \geq 0$


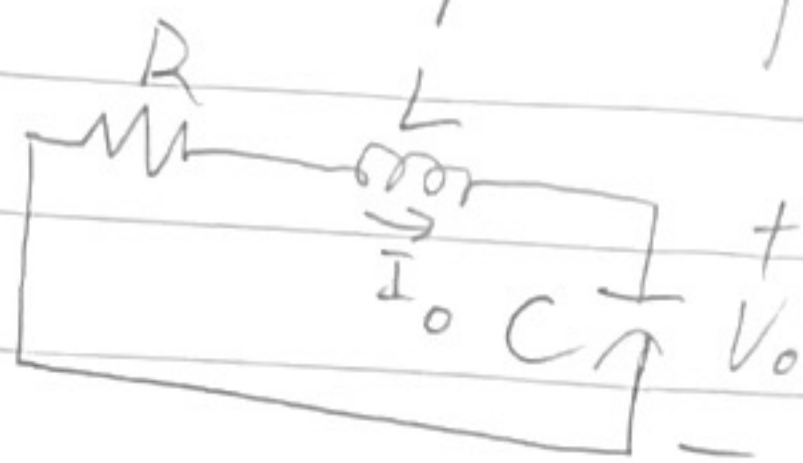
## Natural Response for Series RLC circuit



We use current because current is the same through all the circuit

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$\alpha = \frac{R}{2L} \quad \omega_0 = \sqrt{\frac{1}{LC}} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$\alpha^2 > \omega_0^2 : \text{overdamped} \quad I(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\alpha^2 < \omega_0^2 : \text{underdamped} \quad I(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

$$\alpha^2 = \omega_0^2 : \text{critically damped} \quad I(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

## Duality

③ formula for both ~~circuits~~ circuit is  $\omega_0 = \sqrt{\frac{1}{LC}}$

However, formula for  $\omega_d$  differs:

$$\text{parallel} : \omega_d = \sqrt{\alpha^2 - \omega_0^2}$$

$$\text{series} : \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

④ Natural response for parallel:

$$\text{describing} : \frac{d^2 V(t)}{dt^2} + \frac{1}{RC} \frac{dV(t)}{dt} + \frac{1}{LC} V(t) = 0$$

$$\text{char} : s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

Natural response for series:

$$\text{describing} : \frac{d^2 I(t)}{dt^2} + \frac{R}{L} \frac{dI(t)}{dt} + \frac{1}{LC} I(t) = 0$$

$$\text{char} : s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$